```
* SPICE export by:  S-Edit 16.01
* Export time:      Sun Oct 18 20:41:25 2026
* Design:           mux2
* Cell:             Cell0
* Interface:        view0
* View:             view0
* View type:        connectivity
* Export as:        top-level cell
* Export mode:      hierarchical
* Exclude empty cells: yes
* Exclude .model:   no
* Exclude .end:     no
* Exclude simulator commands:     no
* Expand paths:     yes
* Wrap lines:       no
* Root path:        C:\New folder\mux2
* Exclude global pins:   no
* Exclude instance locations: no
* Control property name(s): SPICE

********* Simulation Settings - General Section *********

***** Top Level *****
MNMOS_1 N_5 B N_1 0 NMOS W=270n L=180nAS=243f PS=2.34uAD=243f PD=2.34u $ $x=-2700 $y=-600 $w=400
$h=600
MNMOS_2 N_5 C N_2 0 NMOS W=270n L=180nAS=243f PS=2.34uAD=243f PD=2.34u $ $x=-800 $y=-600 $w=400
$h=600
MNMOS_3 N_1 N_4 Gnd 0 NMOS W=270n L=180nAS=243f PS=2.34uAD=243f PD=2.34u $ $x=-2700 $y=-1600
$w=400 $h=600
MNMOS_4 N_2AGnd 0 NMOS W=270n L=180nAS=243f PS=2.34uAD=243f PD=2.34u $ $x=-800 $y=-1600 $w=400
$h=600
MNMOS_5 N_4AGnd 0 NMOS W=270n L=180nAS=243f PS=2.34uAD=243f PD=2.34u $ $x=-7500 $y=-800 $w=400
$h=600
MNMOS_6 Out N_5 Gnd 0 NMOS W=270n L=180nAS=243f PS=2.34uAD=243f PD=2.34u $ $x=1100 $y=-200
$w=400 $h=600
MPMOS_1 N_3 B Vdd Vdd PMOS W=810n L=180nAS=729f PS=3.42uAD=729f PD=3.42u $ $x=-2400 $y=2100
$w=400 $h=600
MPMOS_2 N_3 N_4 Vdd Vdd PMOS W=810n L=180nAS=729f PS=3.42uAD=729f PD=3.42u $ $x=-900 $y=2100
$w=400 $h=600
MPMOS_3 N_5 C N_3 Vdd PMOS W=810n L=180nAS=729f PS=3.42uAD=729f PD=3.42u $ $x=-2400 $y=1100
$w=400 $h=600
MPMOS_4 N_5AN_3 Vdd PMOS W=810n L=180nAS=729f PS=3.42uAD=729f PD=3.42u $ $x=-900 $y=1100 $w=400
$h=600
MPMOS_5 N_4AVdd Vdd PMOS W=810n L=180nAS=729f PS=3.42uAD=729f PD=3.42u $ $x=-7500 $y=200
$w=400 $h=600
MPMOS_6 Out N_5 Vdd Vdd PMOS W=810n L=180nAS=729f PS=3.42uAD=729f PD=3.42u $ $x=1100 $y=800
$w=400 $h=600

********* Simulation Settings -Analysis Section *********
.lib "C:\Users\mahak\Downloads\Tanner_v16\Tanner_v16\BPTM_Models files\180nm.md"
Vss Vdd Gnd 1.8
VaAGnd PULSE (0 1.8 0 0.01n 0.01n 10n 20n)
Vb B Gnd PULSE (0 1.8 0 0.01n 0.01n 20n 40n)
Vc C Gnd PULSE (0 1.8 0 0.01n 0.01n 40n 60n)

.tran 0.01n 100n
.power Va
.power Vb
.power Vc
.measure tran delay1 trig v(A) val=0.9 rise=2 targ v(Out) val=0.9 fall=2
.measure tran delay2 trig v(B) val=0.9 rise=2 targ v(Out) val=0.9 fall=2
.measure tran delay3 trig v(C) val=0.9 rise=2 targ v(Out) val=0.9 fall=2
```

.print v(A) v(B) v(C) v(Out)

********* Simulation Settings -Additional SPICE Commands *********

.end